

## Lab Exercise 4

### Objectives

1. Design a simple voltage regulator circuit using a zener diode.
2. Contrast the performance of this circuit with an IC voltage regulator.
3. Check the noise performance of the circuit

### Reading exercise

Please read about filter circuits in [https://www.electronics-tutorials.ws/diode/diode\\_7.html](https://www.electronics-tutorials.ws/diode/diode_7.html)

Viva questions will be based on the lab and reading exercise

With a proper choice of rectifier and filter circuits, the AC voltage should now be a 15V DC voltage. Hence a DC to DC step down voltage circuit is required to convert the 15V DC to a 5V DC. Further, fluctuations in the load at the output of the power supply or due to the AC power supply can still result in occasional spikes in the DC output. In order to provide a constant 5V DC output voltage, we use a voltage regulator circuit at the output of the filter. A simple voltage regulator circuit is shown below in Fig.1.

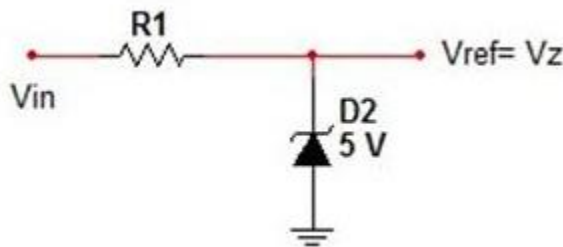


Fig.1. Voltage regulator circuit with zener diode (web link)

The input voltage is fed to a resistor connected to a shunt zener diode. A zener diode is a special type of diode that is operated in the reverse direction when it is used in a voltage regulator. When operated in the reverse bias, the diode maintains a constant voltage across the diode irrespective of the diode current (provided the current is above the minimum breakdown current and below the maximum current rating). The series resistor connected to the zener diode is used to limit the diode current. The load is connected in parallel to the zener diode so that the voltage across the diode is constant irrespective of the value of the load. One problem with zener diode stabiliser circuits is that the diode can sometimes generate electrical noise on top of the DC supply as it tries to stabilise the voltage. Hence, a large value decoupling capacitor should be connected across the zener's output for additional smoothing. We will not build the regulator circuit. Instead we will use a previously fabricated integrated circuit (IC). An IC is a set of electronic circuits that have been fabricated on a semiconductor material. Specifically, we choose the IC7805 circuit.

### Lab exercise

1. Connect a DC input of 15V, a resistor of 1k $\Omega$  and a zener diode rated at 5V . Connect a load resistor  $R_L$  across the diode. Draw this circuit in LTSpice & run transient simulation.
2. Insert a DC input of 15V to the regulator circuit and measure the output voltage across  $R_L$ . Vary  $R_L$  from 100 $\Omega$  to 5K $\Omega$  and note how the output voltage is changing (.op).
3. Now connect the voltage regulator circuit at the load of rectifier circuit with smoothing filter ( $C=2200\mu F$ ) and repeat the study of the previous step.(transient)
4. Now instead of the zener circuit shown in Fig.1, we will consider the Spice model of an IC7805 circuit and connect it to the input DC excitation and output load  $R_L$ .
5. Repeat the tests from step. 2 and step. 3.

6. Turn off source excitation and perform a noise analysis on the circuit at the output up to 10KHz.
7. Introduce a smoothing capacitor at the output of the IC7805 in parallel to the load. Change the capacitor from 5uF to 500uF and observe the noise performance of the resulting circuit.