



**INDRAPRASTHA INSTITUTE *of*  
INFORMATION TECHNOLOGY  
DELHI**

Department  
of  
Electronics & Communication Engineering

Circuit Theory and Devices

Dr. Shobha Sundar Ram

Lab\_1: Transformer  
Week\_1

Mohammad Shariq  
2020220  
27-Sep-2021

---

## **Objective:** Simulation of Transformer in LTspice and some analysis

### **Components Used:**

- LTSpice as Simulation Software
- Transformer(Ideal Transformer for making a non-ideal Transformer)
- Voltage Source
- Resistors

### **Diagram:**

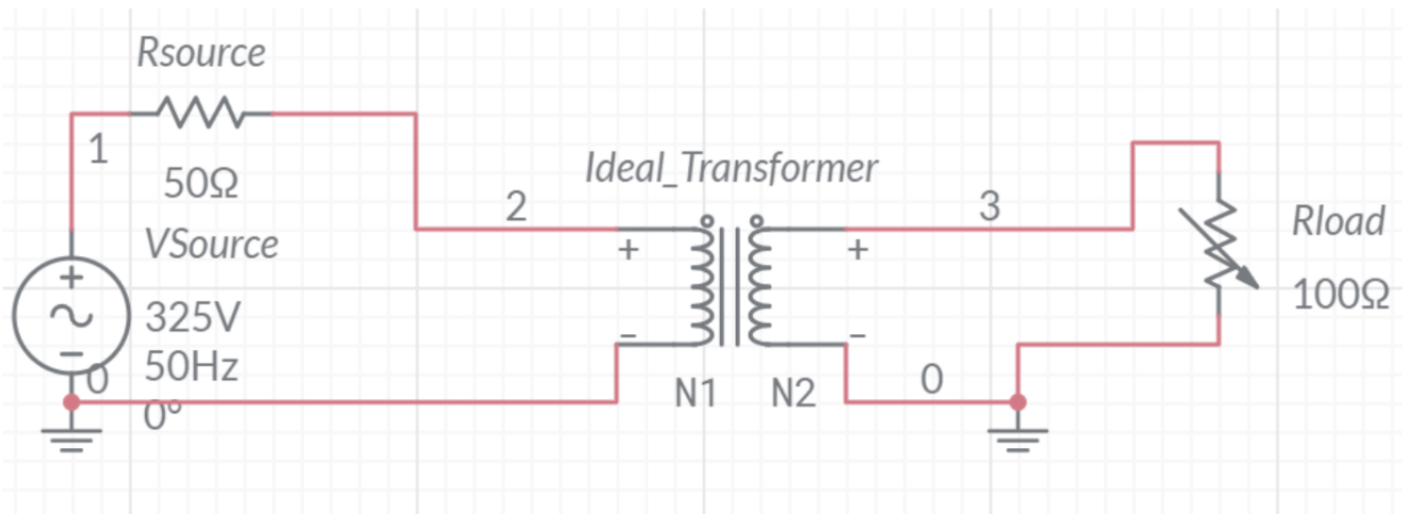


Fig.4 Simulation of the power supply with ideal transformer circuit

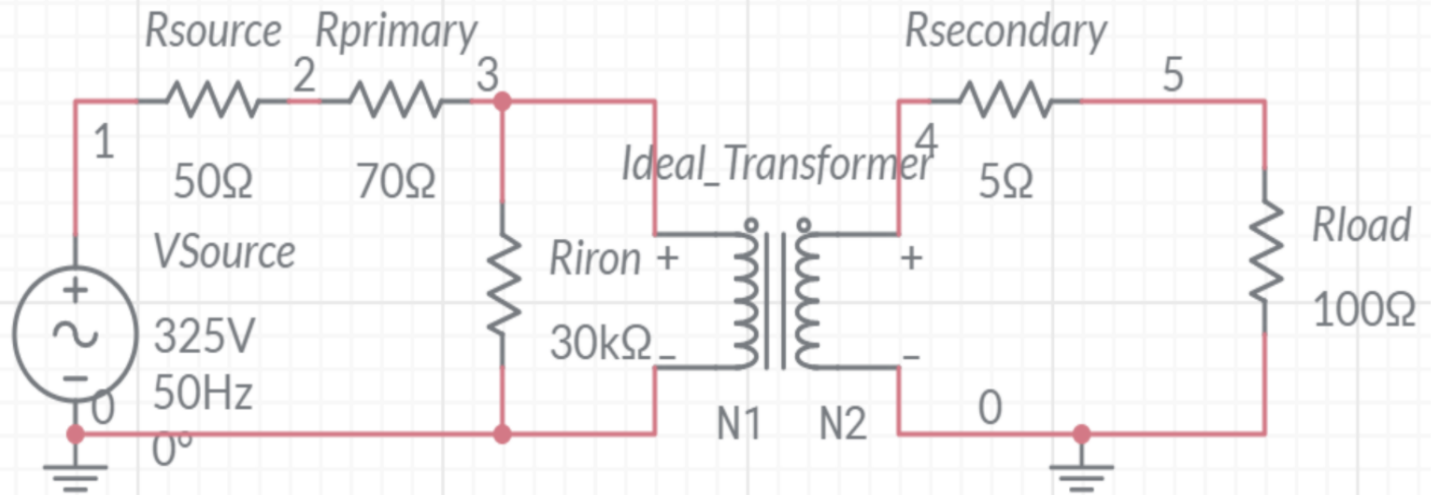


Fig 5 : Simulation of the Non-ideal transformer circuit

### Theoretical Calculation:

- For Ideal Transformer :

$$V_{rms} = V_{source} = \frac{V_{peak}}{\sqrt{2}} = \frac{325 \text{ V}}{\sqrt{2}} = 229.8097 \text{ V}$$

$$I_{rms} = I_{source} = \frac{I_{peak}}{\sqrt{2}} = \frac{13.75 \text{ mA}}{\sqrt{2}} = \frac{13.79 \text{ mA}}{\sqrt{2}} = 9.751 \text{ mA} \approx 0.009751 \text{ A}$$

$$P_{source} = V_{source} \times I_{source} = 229.8097 \times 0.009751 = 2.24087 \text{ W}$$

$$V_{load} = \frac{V_{load-peak}}{\sqrt{2}} = \frac{21.09 \text{ V}}{\sqrt{2}} = 14.9128 \text{ V}$$

$$I_{load} = \frac{I_{load-peak}}{\sqrt{2}} = \frac{210.46 \text{ mA}}{\sqrt{2}} = 149.262 \text{ mA} = 0.149262 \text{ A}$$

$$P_{load} = V_{load} \times I_{load} = 14.912 \text{ V} \times 0.14926 \text{ A} \\ = 2.2257 \text{ W}$$

$$\text{Efficiency (non-ideal)} = \frac{P_{load}}{P_{source}} \times 100 \%$$

$$= \frac{2.2257}{2.24087} \times 100$$

$$= 0.993230 \times 100$$

$$= 99.3230 \%$$

- For NON\_Ideal Transformer:

$$V_{rms} = V_{source} = \frac{V_{peak}}{\sqrt{2}} = \frac{325}{\sqrt{2}} = 230 \text{ V.}$$

$$I_{rms} = I_{source} = \frac{I_{peak}}{\sqrt{2}} = \frac{23.80 \text{ mA}}{\sqrt{2}} = 16.829 \text{ mA.}$$

$$P_{source} = V_{source} \times I_{source} = 230 \times 0.016829 = 3.8706 \text{ W}$$

$$V_{primary} = (1.657/\sqrt{2}) \text{ V} = 1.1716 \text{ V}$$

$$I_{primary} = \frac{23.74 \text{ mA}}{\sqrt{2}} = 16.786 \text{ mA}$$

$$P_{primary} = 1.1716 \times 0.016786 = 0.02880 \text{ W}$$

$$V_{load} = (19.98/\sqrt{2}) \text{ V} = 14.12092 \text{ V}$$

$$I_{load} = \frac{199.19 \text{ mA}}{\sqrt{2}} = 140.848 \text{ mA.}$$

$$P_{load} = 14.120 \times 0.14084 = 1.9886 \text{ W}$$

$$\text{Eff} = \frac{P_{load}}{P_{source}} = \frac{1.9886 \times 100}{3.8706} = 0.51327 = \underline{\underline{51.327\%}}$$

$$\epsilon_1 = \frac{P_{load}}{P_{primary}} = \frac{1.9886}{0.0288} = 69.0486$$

PAGE :  
DATE : / /

## Observations:


- FOR Ideal-Transformer::


S.No	Secondary R <sub>LOAD</sub> [Ω]	V <sub>source</sub> [V]	I <sub>source</sub> [A]	P <sub>source</sub> [W]	V <sub>load</sub> [V]	I <sub>load</sub> [A]	P <sub>load</sub> [W]	Efficiency (P <sub>load</sub> / P <sub>source</sub> )[%]
1	10 <sup>2</sup>	230	9.751 mA	2.2408	14.912	149.26 mA	2.225	99.323
2	10 <sup>3</sup>	230	0.9808 mA	0.2255	14.91	14.97 mA	0.2232	98.98
3	9 × 10 <sup>3</sup>	230	108.067 μA	0.02505	14.98	1.67 mA	0.025	99.80
4	4 × 10 <sup>4</sup>	230	24.37 μA	0.005605	14.97	373.41 μA	0.005589	99.727
5	2 × 10 <sup>5</sup>	230	4.865 μA	0.0011189	14.98	74.75 μA	0.0011185	99.97

● **FOR NON-Ideal-Transformer::**

S.No	Secondary $R_{LOAD} [\Omega]$	$V_{source}$ [V]	$I_{source}$ [A]	$P_{source}$ [W]	$V_{primary}$	$I_{primary}$	$P_{primary}$	$V_{load}$ [V]	$I_{load}$ [A]	$P_{load}$ [W]	Efficiency of Transformer ( $P_{load}/P_{primary}$ )	Efficiency of power source ( $P_{load}/P_{source}$ ) [%]
1	$10^2$	230	$16.879 \text{ mA}$	3.8706	1.1716	$16.78 \text{ mA}$	0.02880	14.12V	$140.84 \text{ mA}$	1.9886	69.0486	51.377 %
2	$10^3$	230	$\frac{12.123 \text{ mA}}{\sqrt{2}}$	1.9719	$\frac{0.850}{\sqrt{2}}$	$\frac{12.120 \text{ mA}}{\sqrt{2}}$	0.005151	$\frac{20.92}{\sqrt{2}}$	$\frac{20.97}{\sqrt{2}} \text{ (mA)}$	0.21934	42.5820	11.123 %
3	$9 \times 10^3$	230	$\frac{10.932 \text{ mA}}{\sqrt{2}}$	1.777	$\frac{0.7653}{\sqrt{2}}$	$\frac{10.92 \text{ mA}}{\sqrt{2}}$	0.004178	$\frac{21.08}{\sqrt{2}}$	$\frac{2.336}{\sqrt{2}} \text{ (mA)}$	0.024621	5.89310	1.3848 %
4	$4 \times 10^4$	230	$\frac{10.798 \text{ mA}}{\sqrt{2}}$	1.7613	$\frac{0.7537}{\sqrt{2}}$	$\frac{10.77 \text{ mA}}{\sqrt{2}}$	0.004058	$\frac{20.96}{\sqrt{2}}$	$\frac{521.57}{\sqrt{2}} \text{ (uA)}$	0.005497	1.35472	0.31209 %
5	$2 \times 10^5$	230	$\frac{10.69 \text{ mA}}{\sqrt{2}}$	1.7437	$\frac{0.7534}{\sqrt{2}}$	$\frac{10.71 \text{ mA}}{\sqrt{2}}$	0.004034	$\frac{21.05}{\sqrt{2}}$	$\frac{105.17}{\sqrt{2}} \text{ (uA)}$	0.0011069	0.27434	0.06348 %

**Plots:**

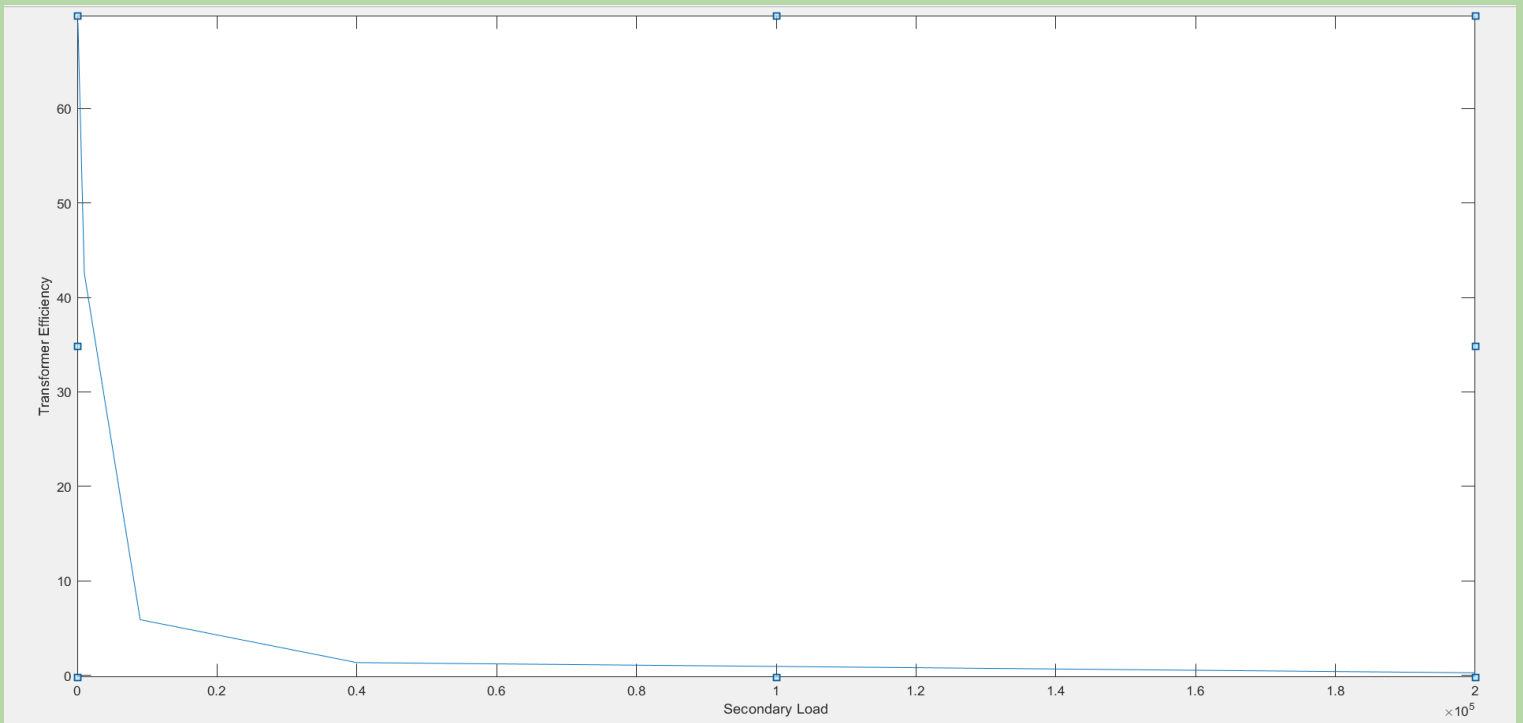

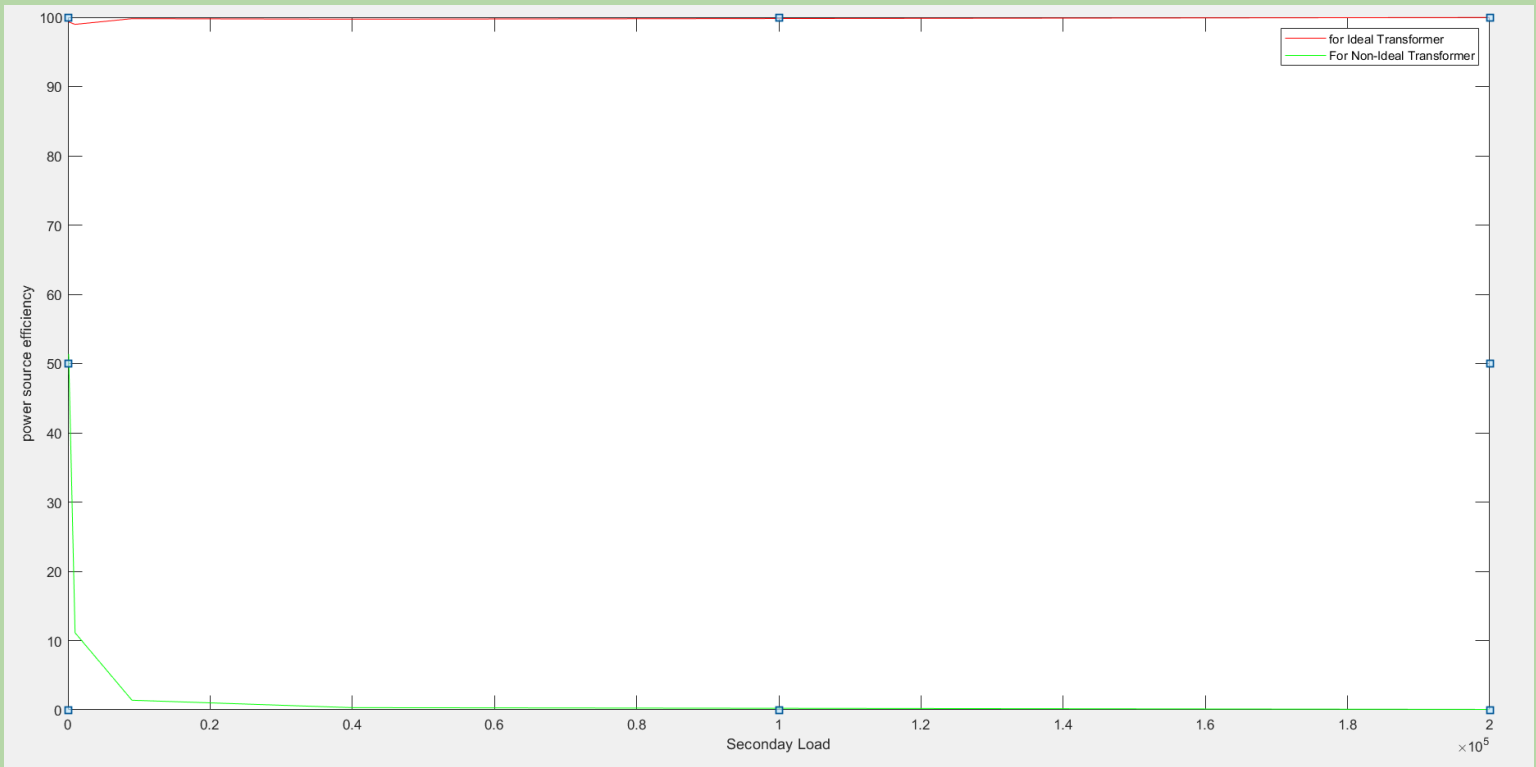

## **Conclusions:**

The suitable range of loads at which the transformer should be operated so that both the efficiencies are within a maximum optimum range are between 100 ohm to 1000 ohm.