



**INDRAPRASTHA INSTITUTE *of*
INFORMATION TECHNOLOGY
DELHI**

Department
of
Electronics & Communication Engineering

Circuit Theory and Devices

Dr. Shobha Sundar Ram

Lab_2: Rectifiers
Week_2

Mohammad Shariq
2020220
06-Oct-2021

Objective:


1. Design of three different types of rectifiers in LTSpice.
2. Explore ways to reduce the ripple in the output voltage.

Components Used:


- LTSpice as Simulation Software
- Transformer
- Diode
- Voltage Source
- Resistors

Diagram:

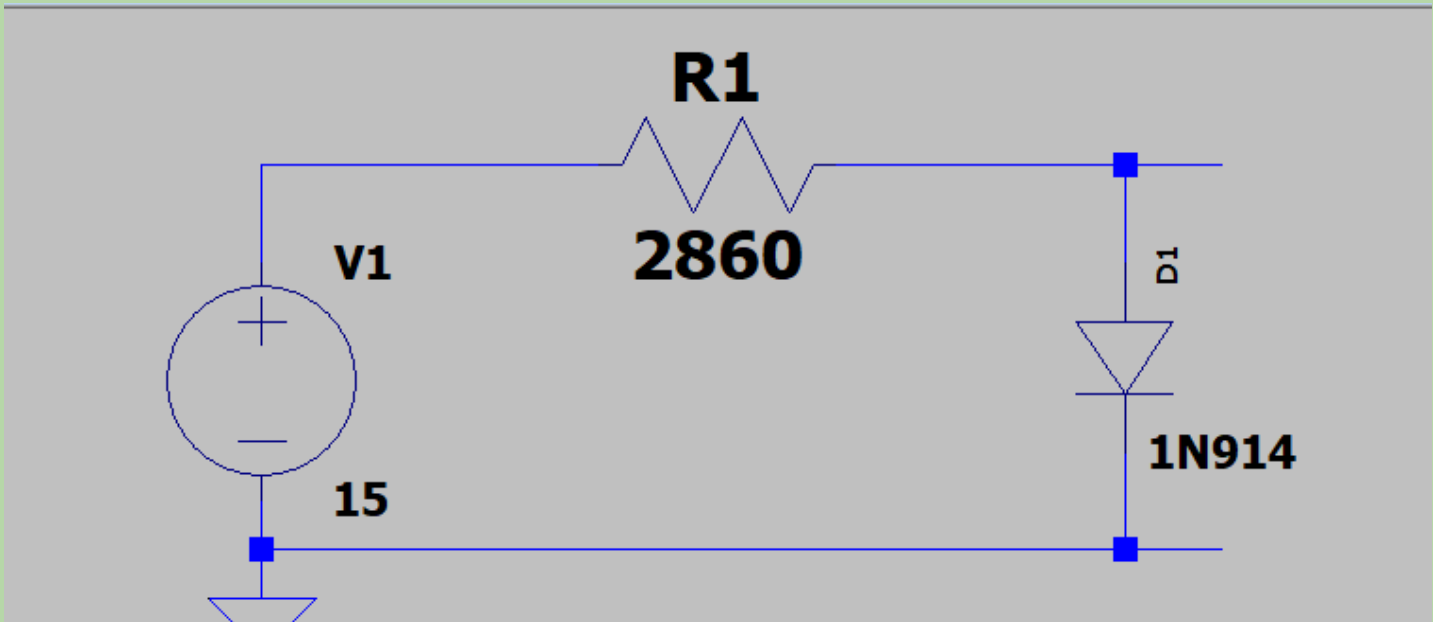
- Limiting Circuit / Diode Clipping Circuit:




- Half-Wave rectifier

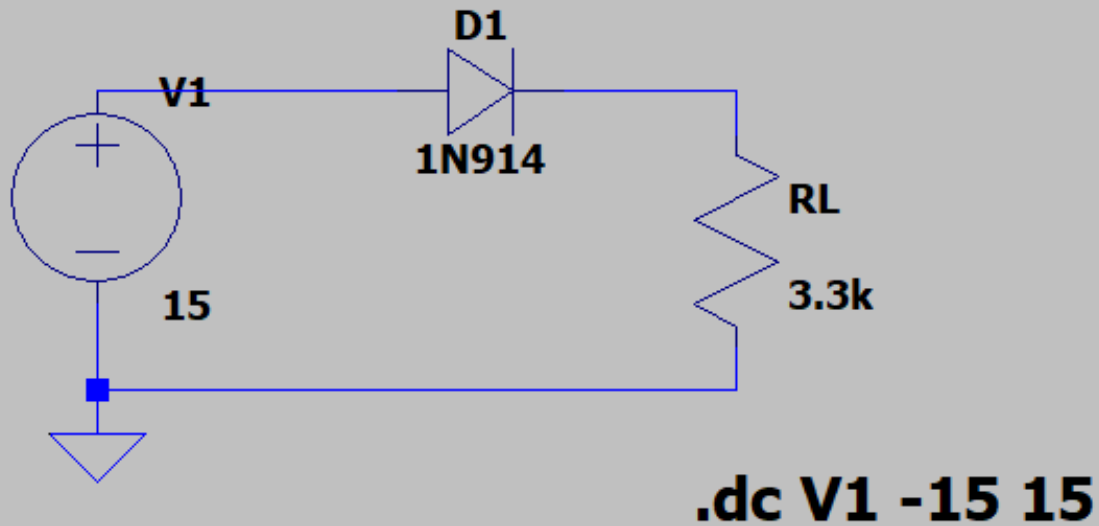

- Center Tapped Full wave rectifier

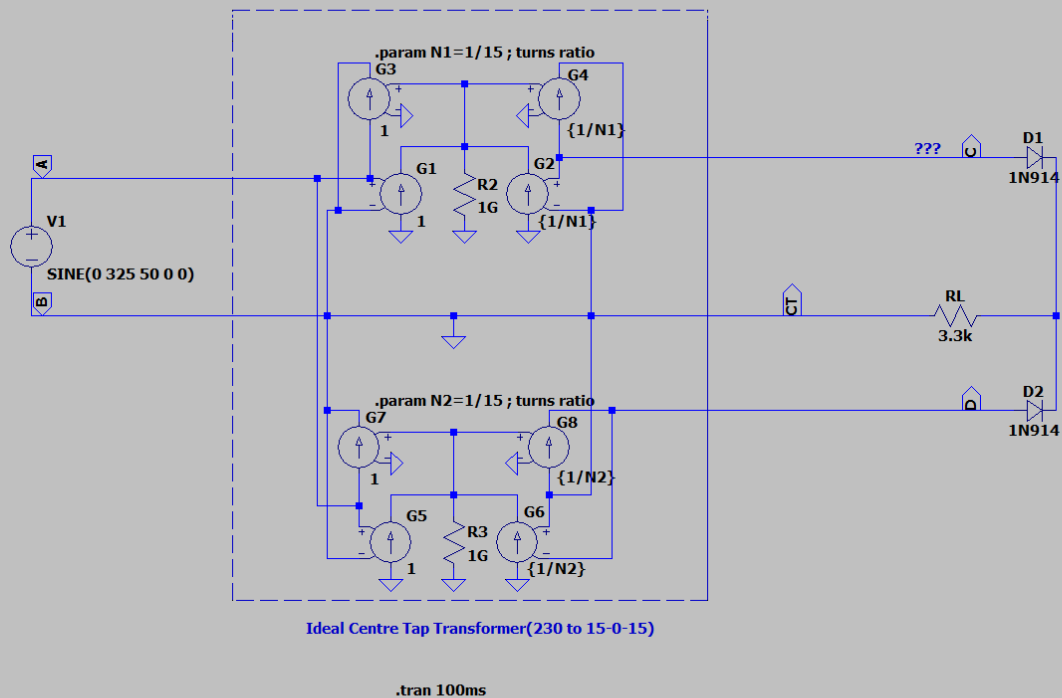


• Full Wave Bridge Rectifier

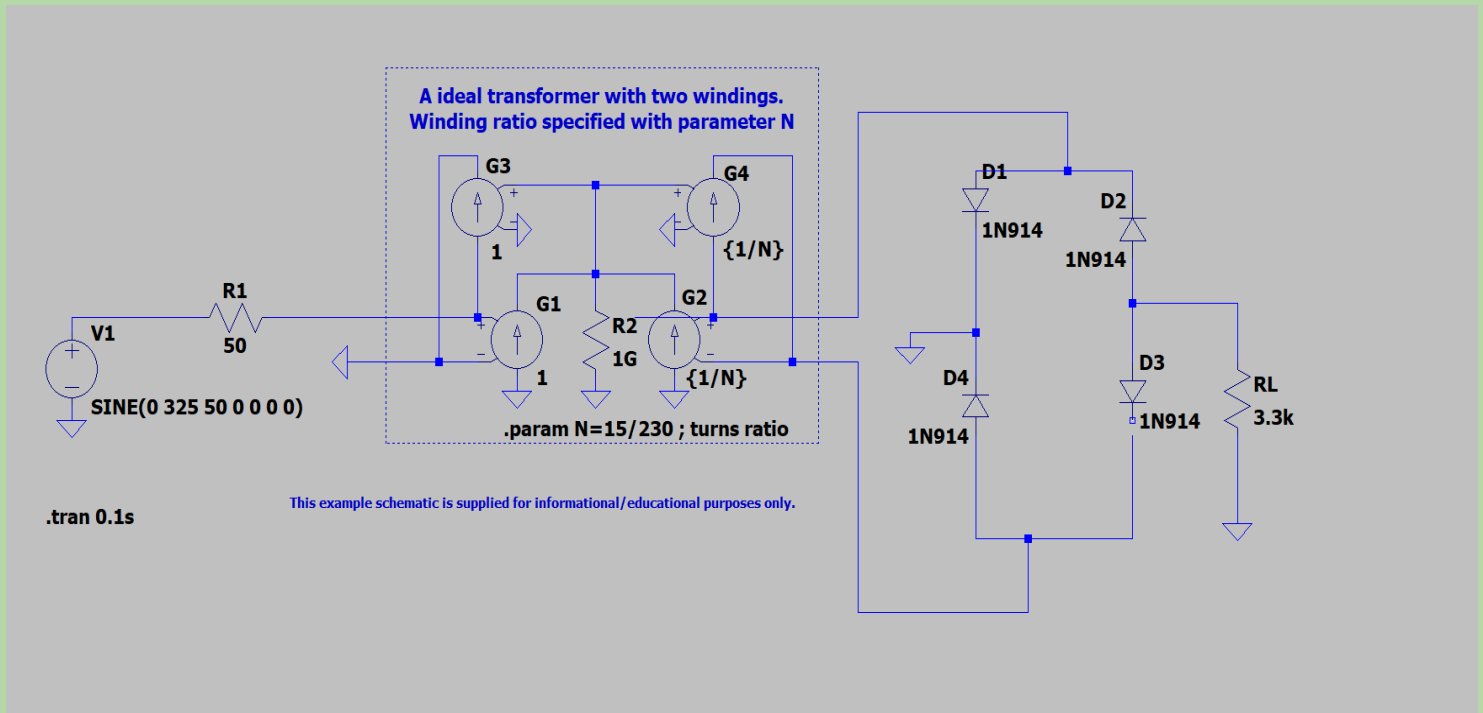

Plots:

• Limiting Circuit / Diode Clipping Circuit:

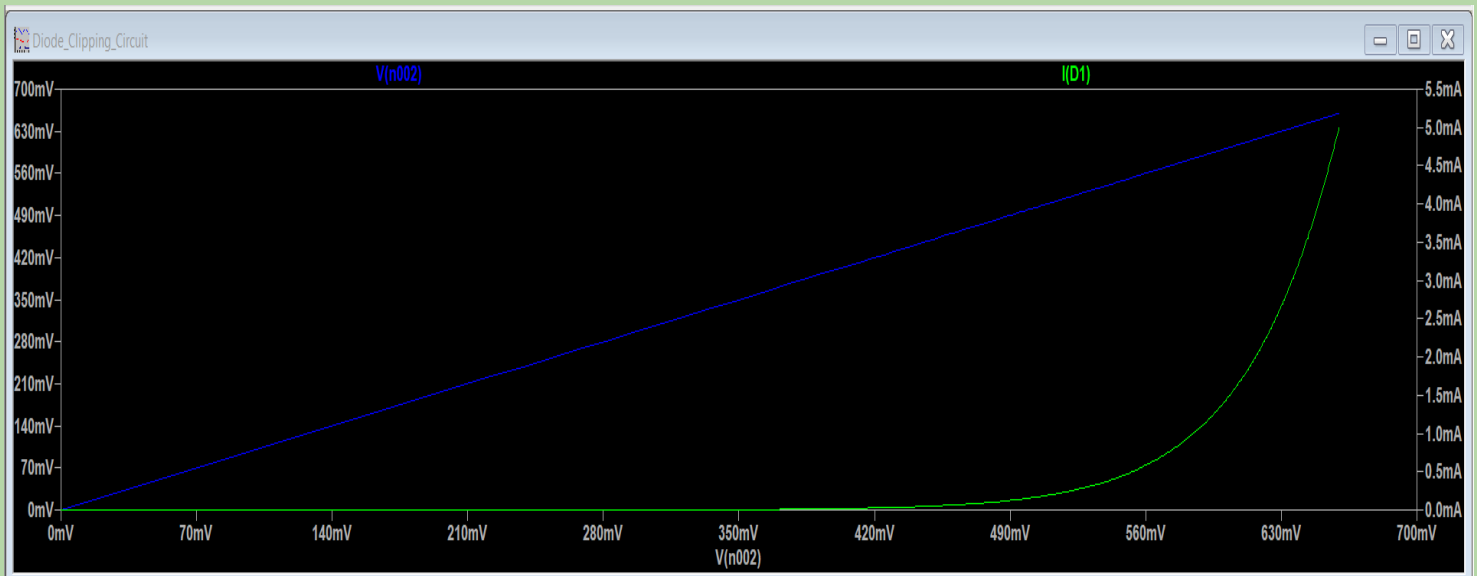
❖ I-V characteristic of the diode (voltage and current across the diode)



- ❖ plot the transfer function (V_{OUT} divided by V_{IN}) of the circuit. Note that the diode voltage is the output voltage



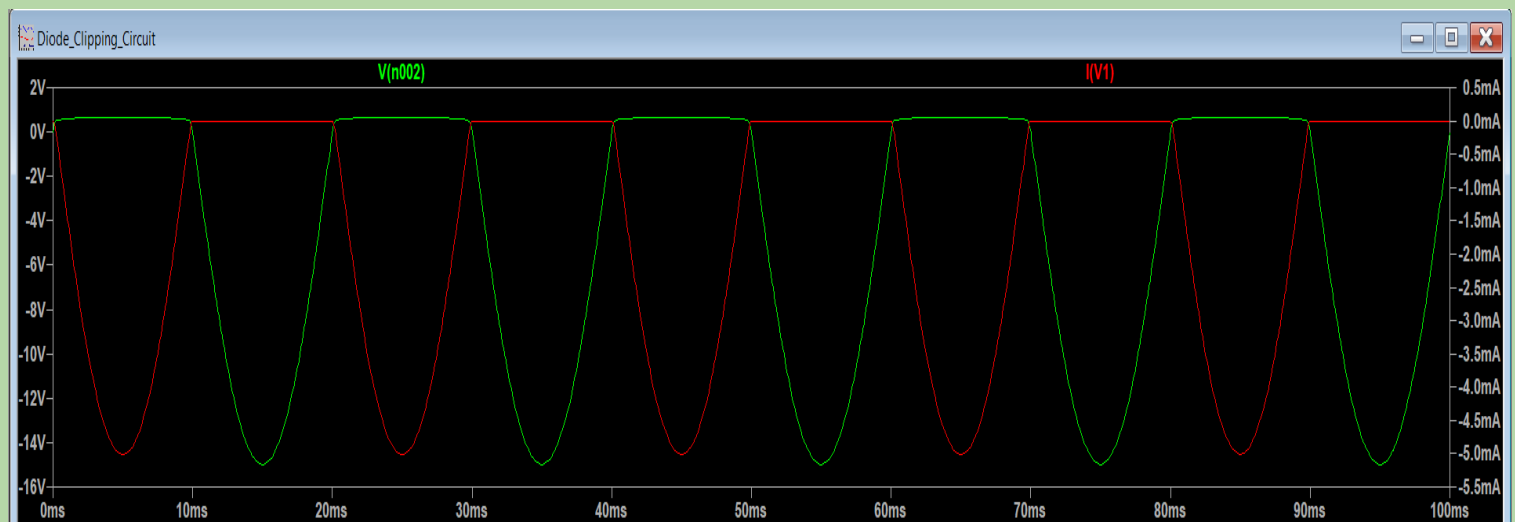- ❖ A transient simulation for the circuit keeping V_{IN} as 15V, 50Hz sinusoidal wave



- **Half-Wave Rectifier**


- ❖ **Diode voltage and diode current**




❖ transfer function (V_{OUT} , divided by V_{IN}) of the circuit. Note that the resistor voltage is the output voltage in this circuit



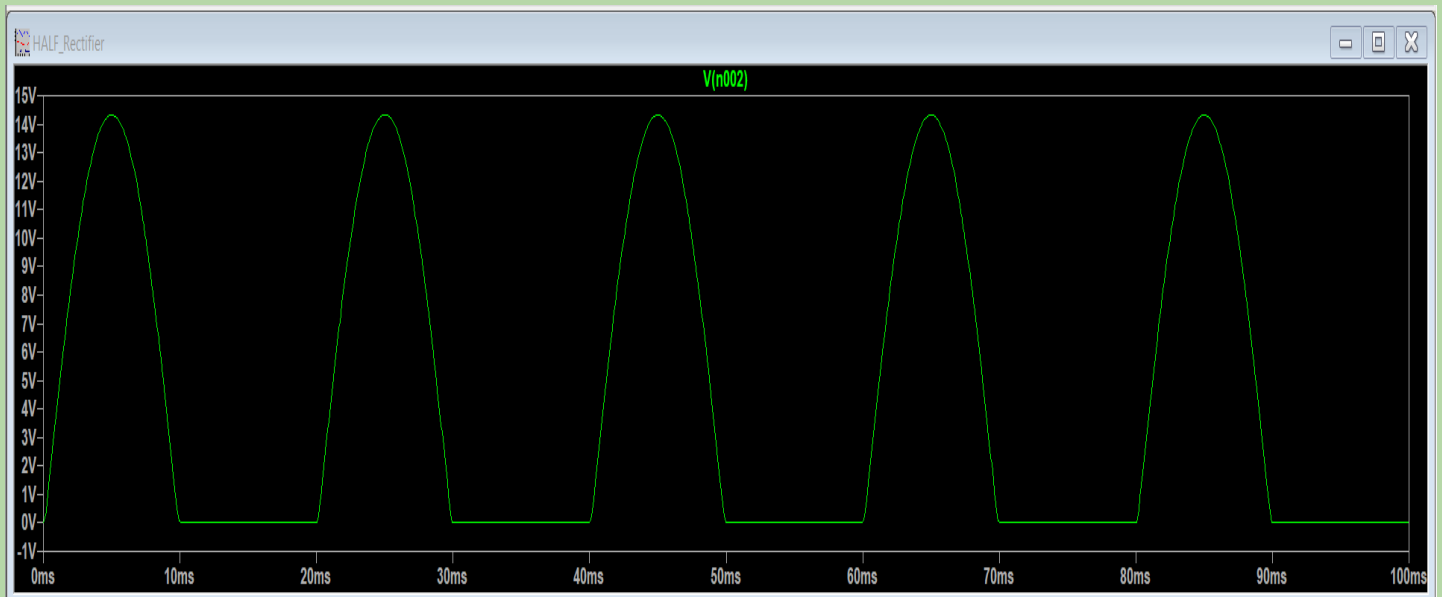- ❖ Replace the DC source with an AC source excitation with an amplitude of 15V and a frequency of 50Hz. Use LTSpice to plot the resistor's voltage across several time cycles using transient simulation.




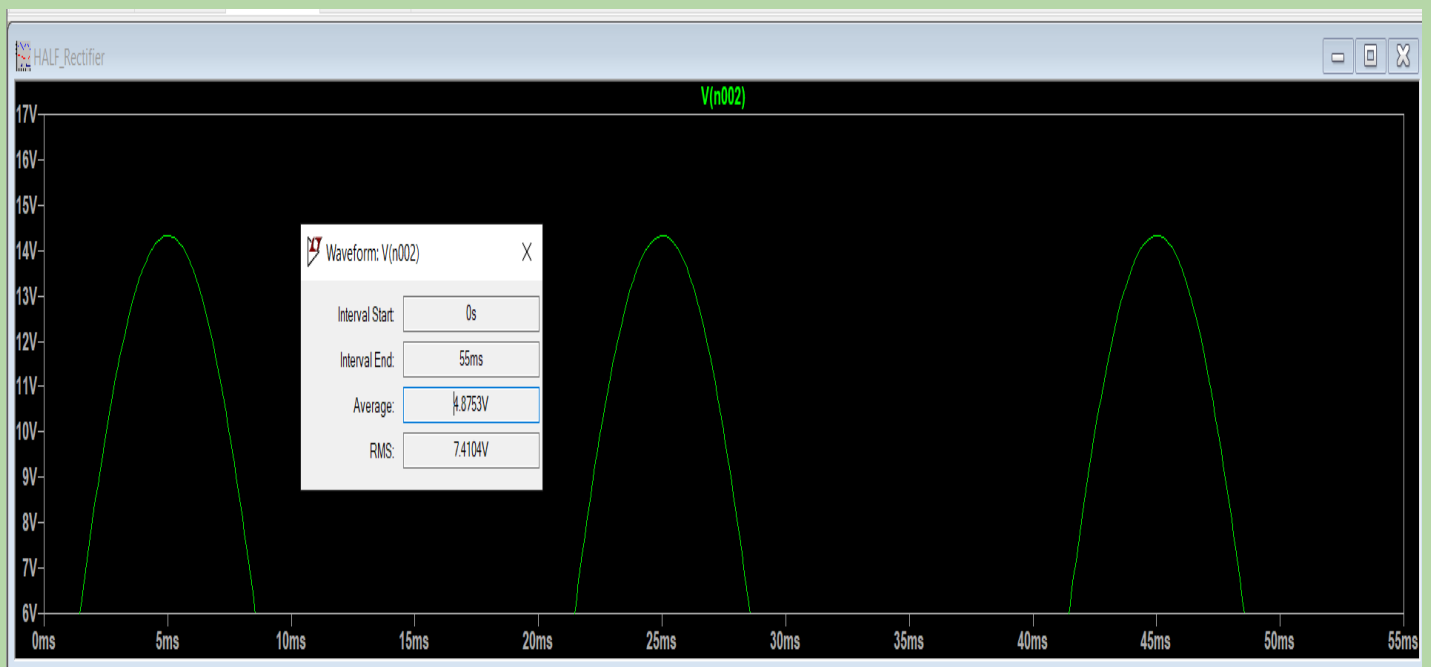- ❖ The time-averaged output voltage, V_{OUT} , across three time cycles




- **Center Tapped Full wave rectifier**

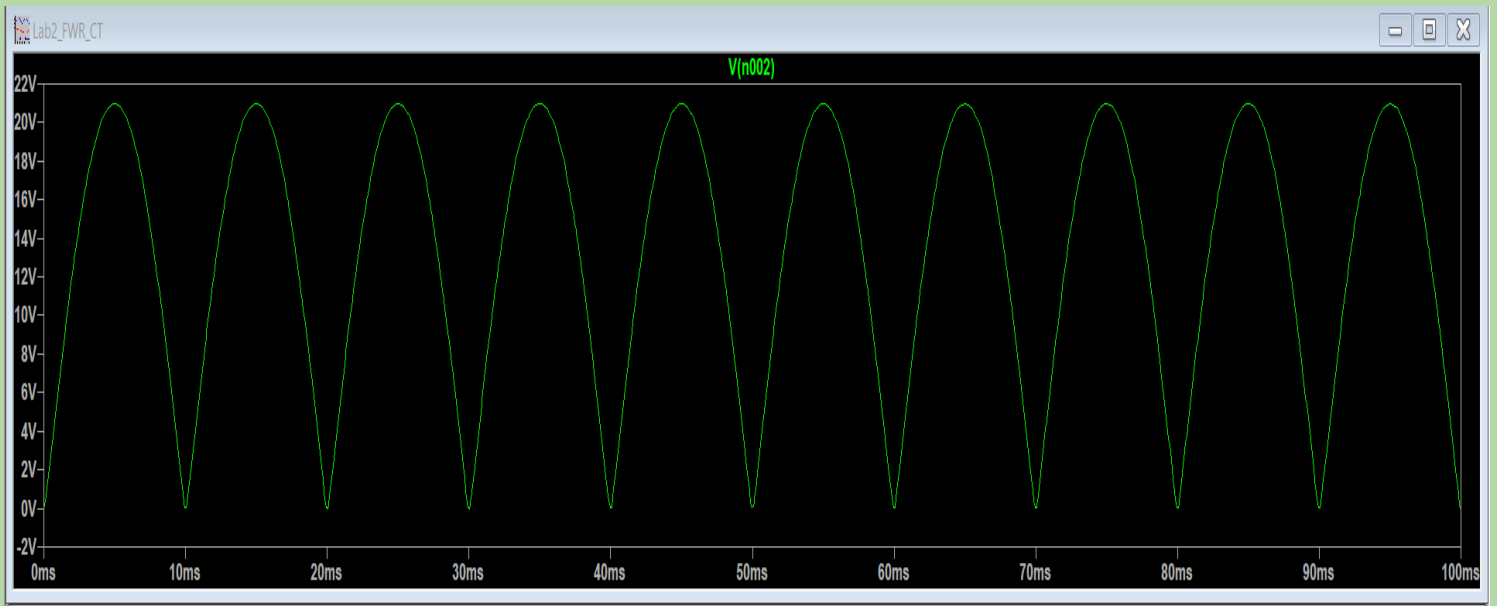- ❖ Use an AC source excitation with an amplitude of 230Vrms and a frequency of 50Hz as the input to the primary of an ideal step down transformer (15:1). Use LTSpice to plot the resistor's voltage across several time cycles using transient simulation




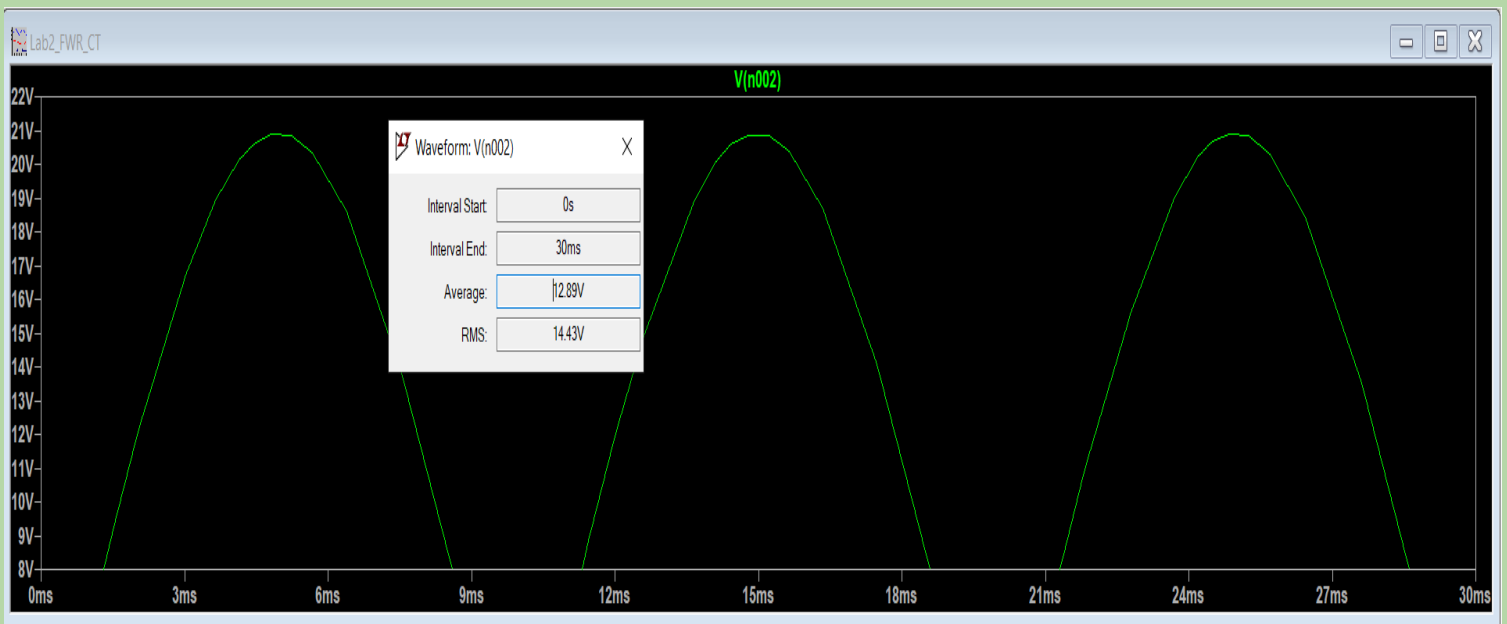- ❖ the time-averaged output voltage across three time cycles




• Full Wave Bridge Rectifier

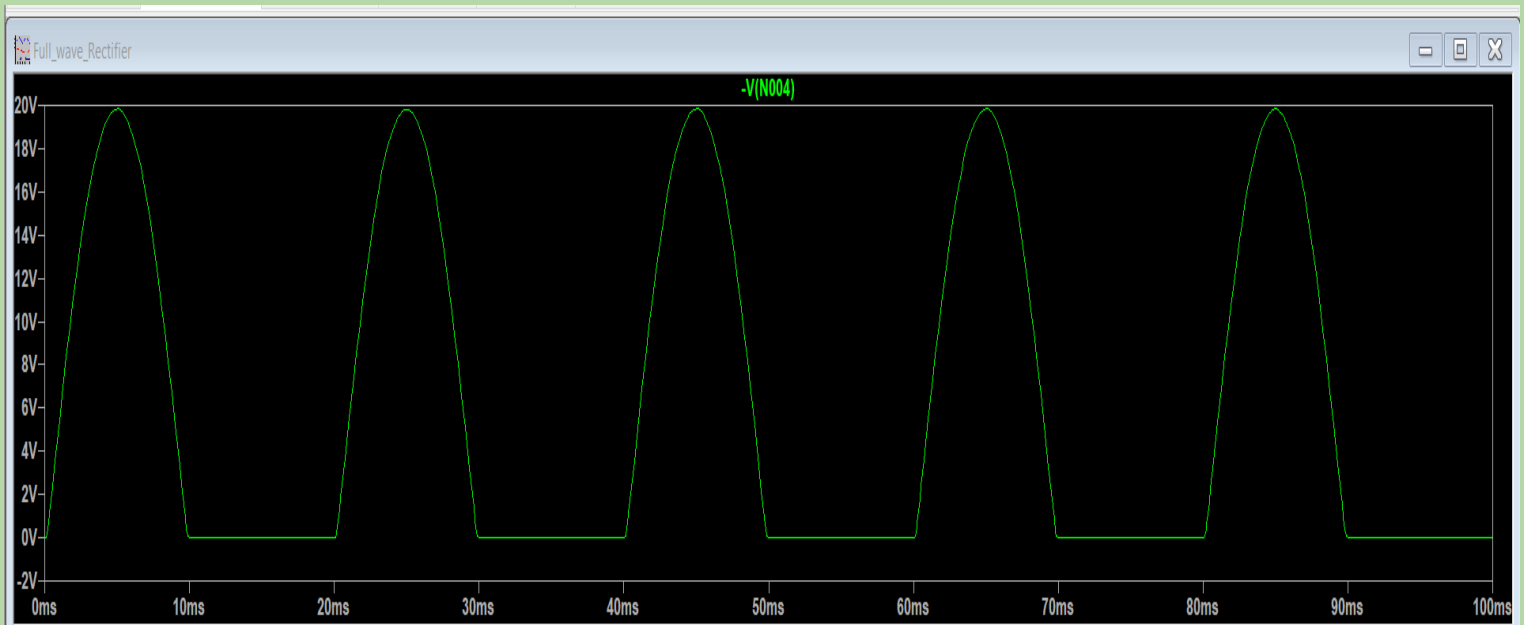- ❖ Use an AC source excitation with an amplitude of 230Vrms and a frequency of 50Hz in the primary of an ideal step down transformer (15:1). Use LTSpice to plot the resistor's voltage across several time cycles using transient simulation



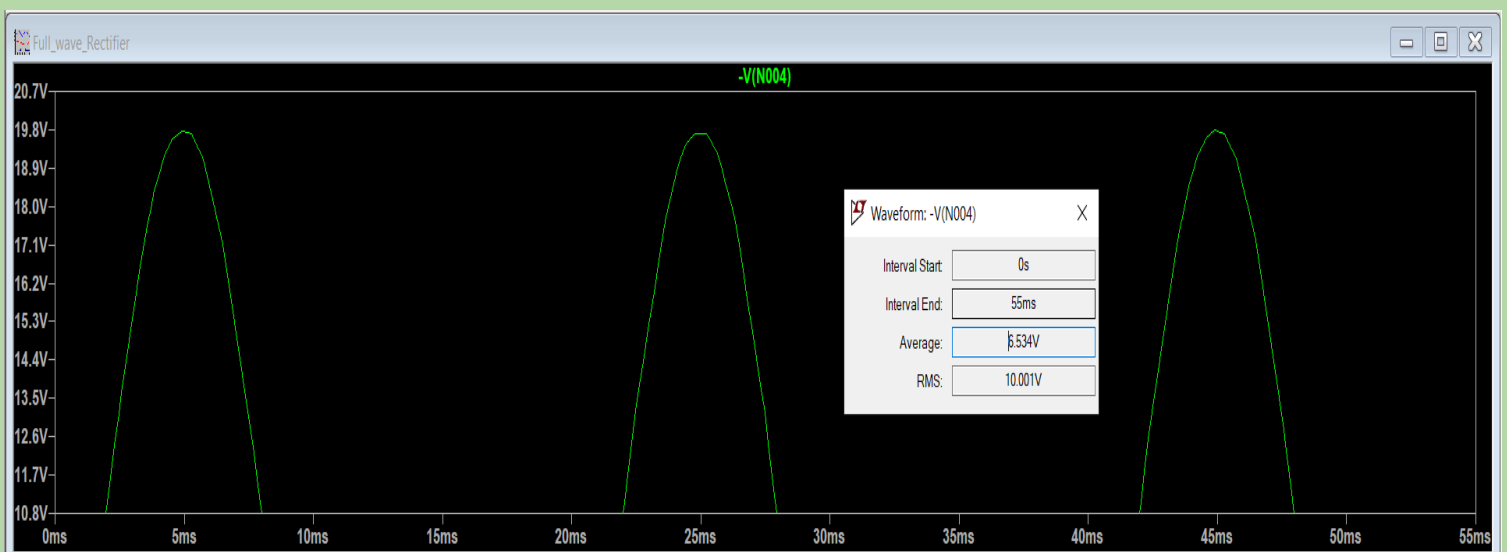- ❖ The time-averaged output voltage across three time cycles



Observations:

- Half-Wave Rectifier
 $V_{avg}=4.8753\text{ V}$
 $V_{rms}=7.4104\text{ V}$
- Center Tapped Full wave rectifier
 $V_{rms}=14.43/1.41=10.2035\text{ V}$
 $V_{avg}=12.84/1.41=9.079\text{ V}$
- Full-wave Bridge Rectifier
 $V_{rms}=10.001/1.41=4.6202\text{ V}$
 $V_{avg}=6.534/1.41=4.6202\text{ V}$

Conclusions:

From the above results we can observe that Center Tapped Full wave Rectifier is giving maximum avg Voltage and max root mean square Voltage Hence we will prefer it for our circuit.